

# Sequential Logic

Jinyang Li

# What we've learnt so far

- Combinatorial logic
  - E.g. Multiplexors (Mux), Decoders
  - Two ways of building a CL
    - Truth table  $\rightarrow$  sum of products circuits
    - ROM
- ALU
  - Compute all operations (+, OR, AND, NOR), multiplexer picks the result
  - Building a 64-bit adder
    - Ripple carry chains together 1-bit adders
    - Carry lookahead

# Today's lesson plan

- Sequential circuit: Memory (state) elements
- Sequential circuit: Finite State Machine


# Two types of logic circuits

- Combinatorial circuit
  - PLA: Truth table  $\rightarrow$  sum of products PLA circuit
  - ROM (read-only memory): Addresses (inputs)  $\rightarrow$  contents (outputs)
- Sequential circuit
  - output is dependent on both input and state (memory elements)

Today's lesson




# Sequential logic requires clock

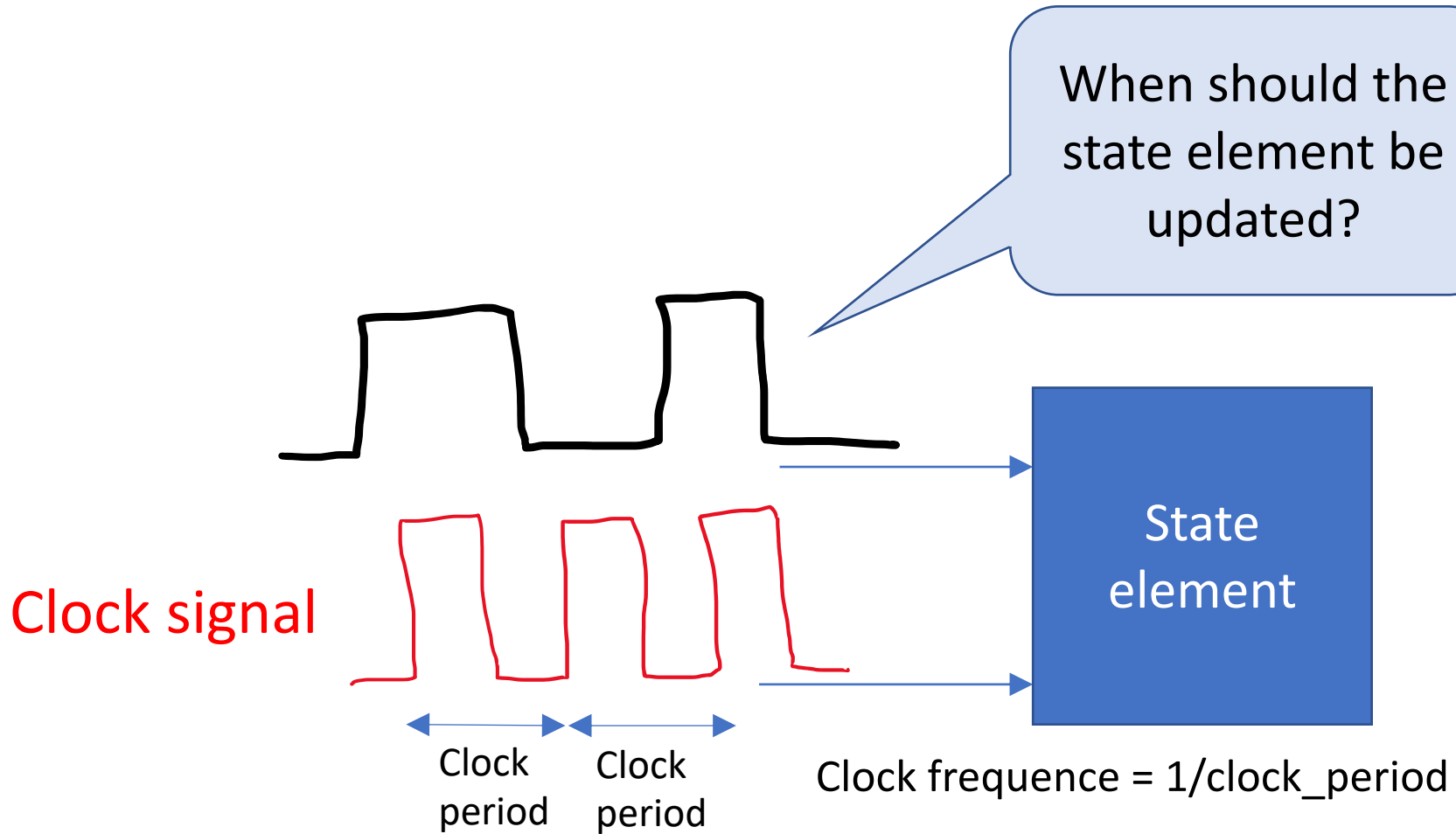

 
# Clocks


- Edge-triggered clocking: state content only changes on active clock edge



# Sequential logic requires clock

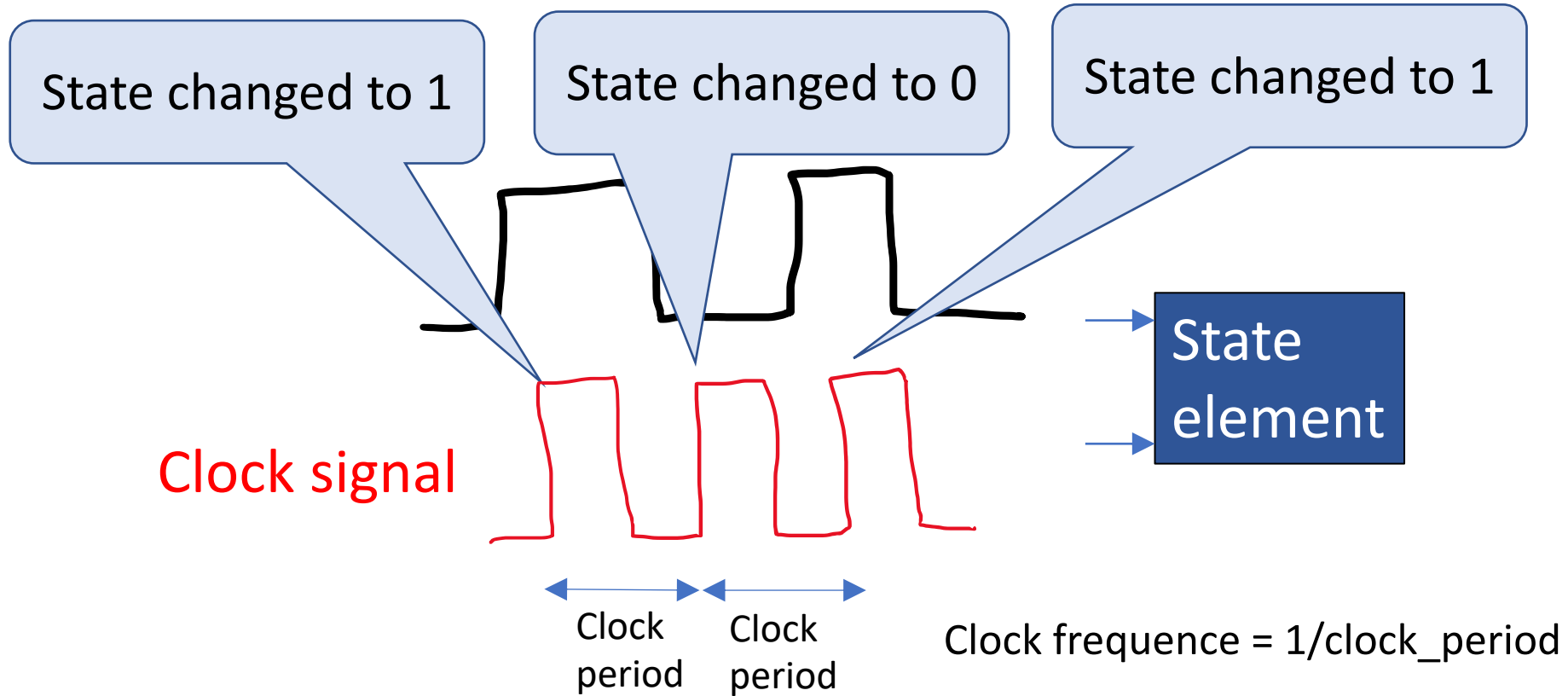


# Sequential logic requires clock

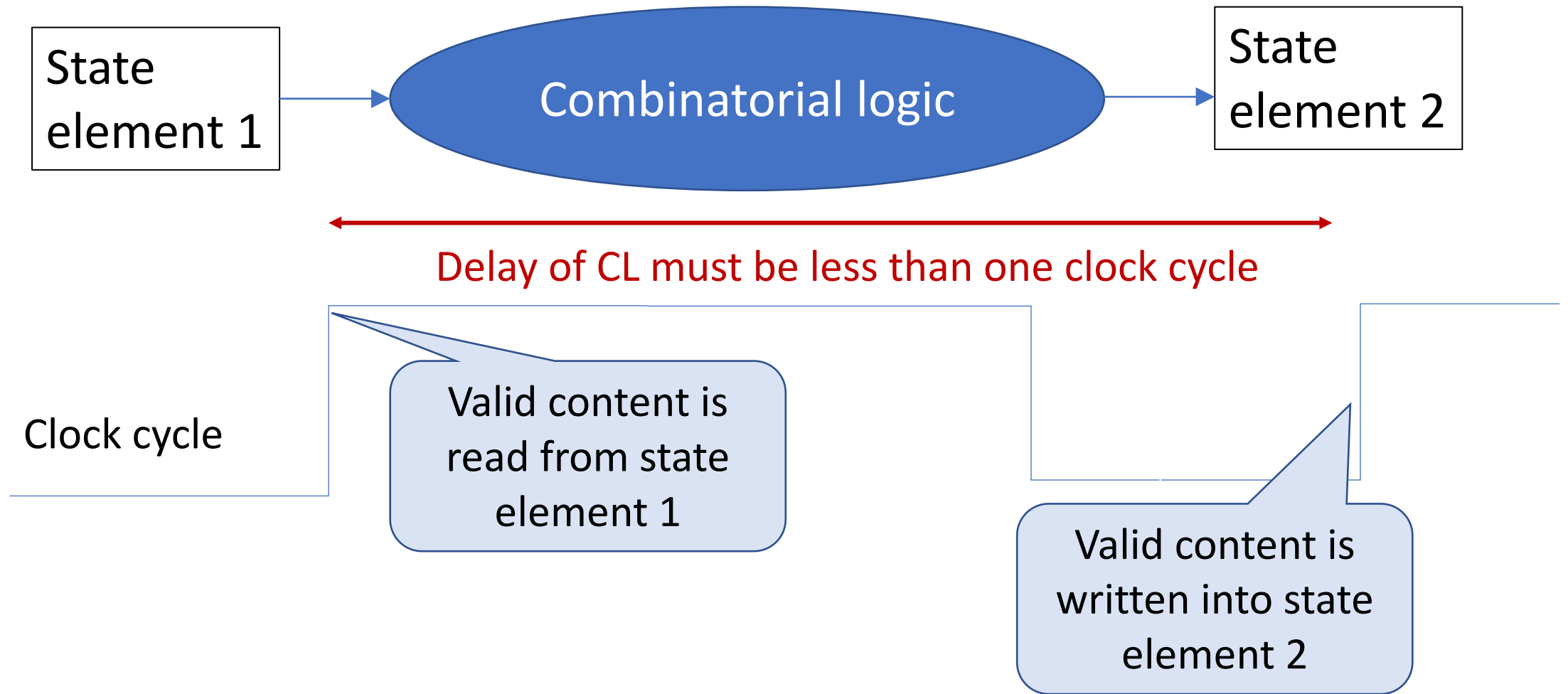




# Sequential logic requires clock

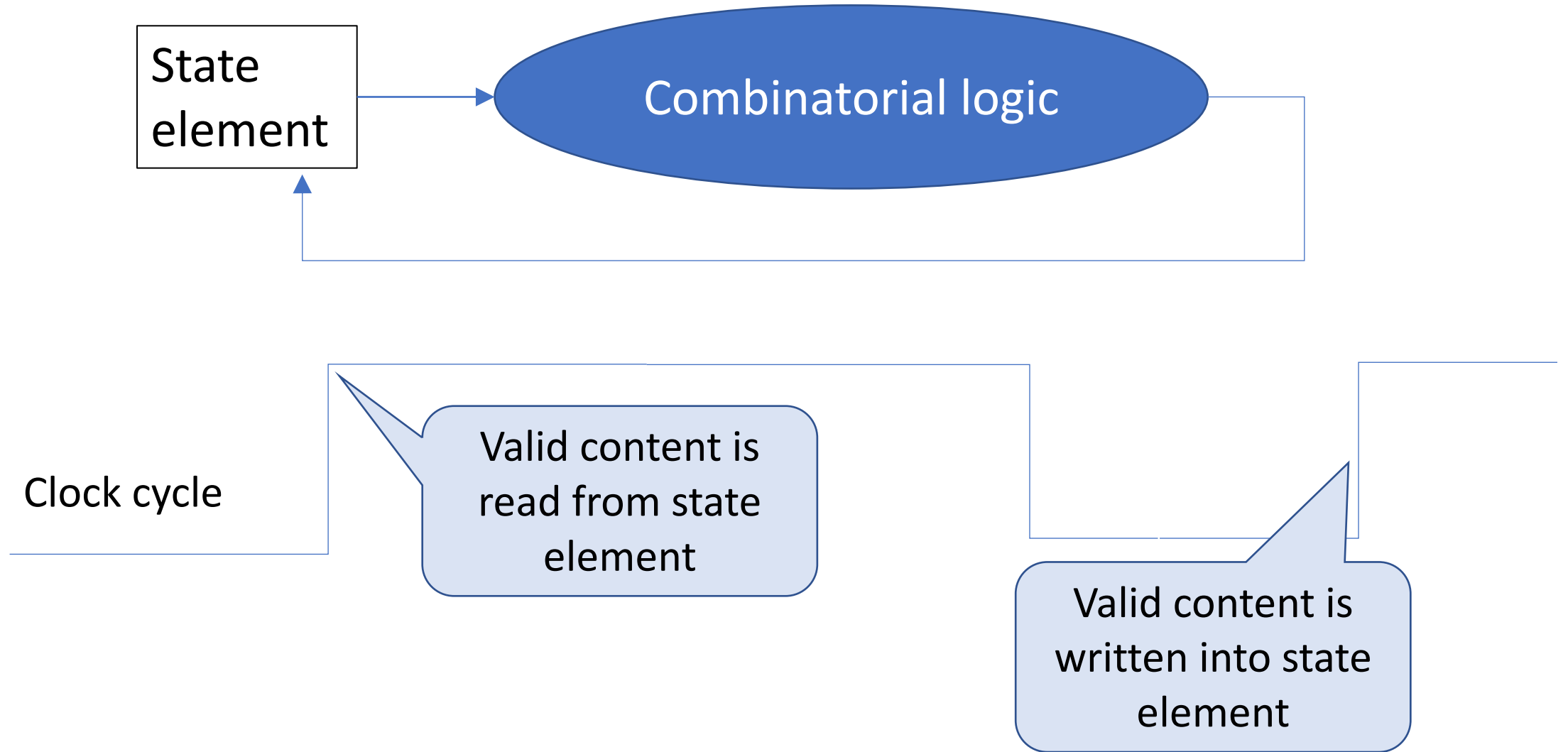


# Memory (state) elements: unlocked S-R Latch

S (set)	R (reset)	
0	0	
1	0	
0	1	
1	1	

 


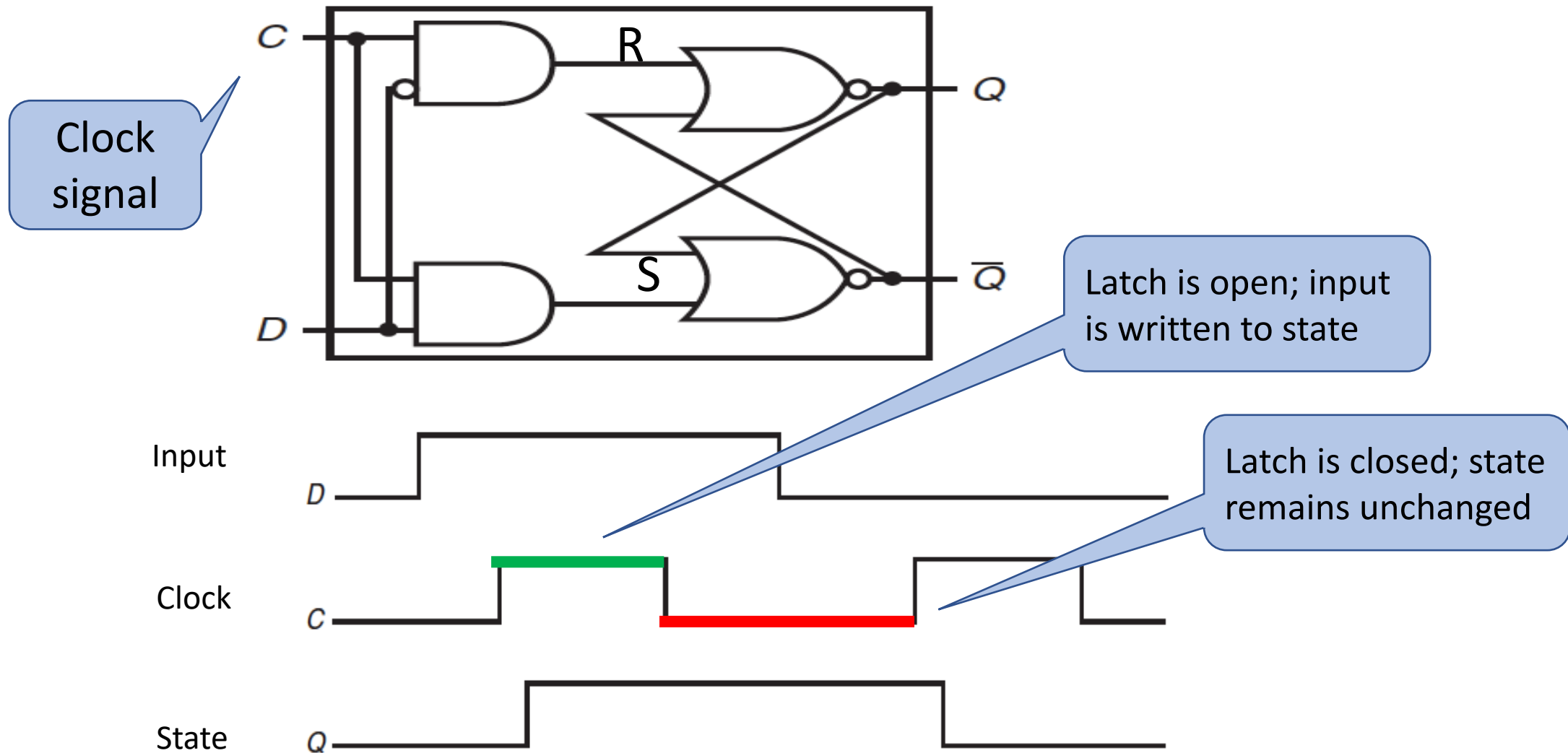
# Memory element: clocked D latch

- D latch: state is changed as long as clock is asserted


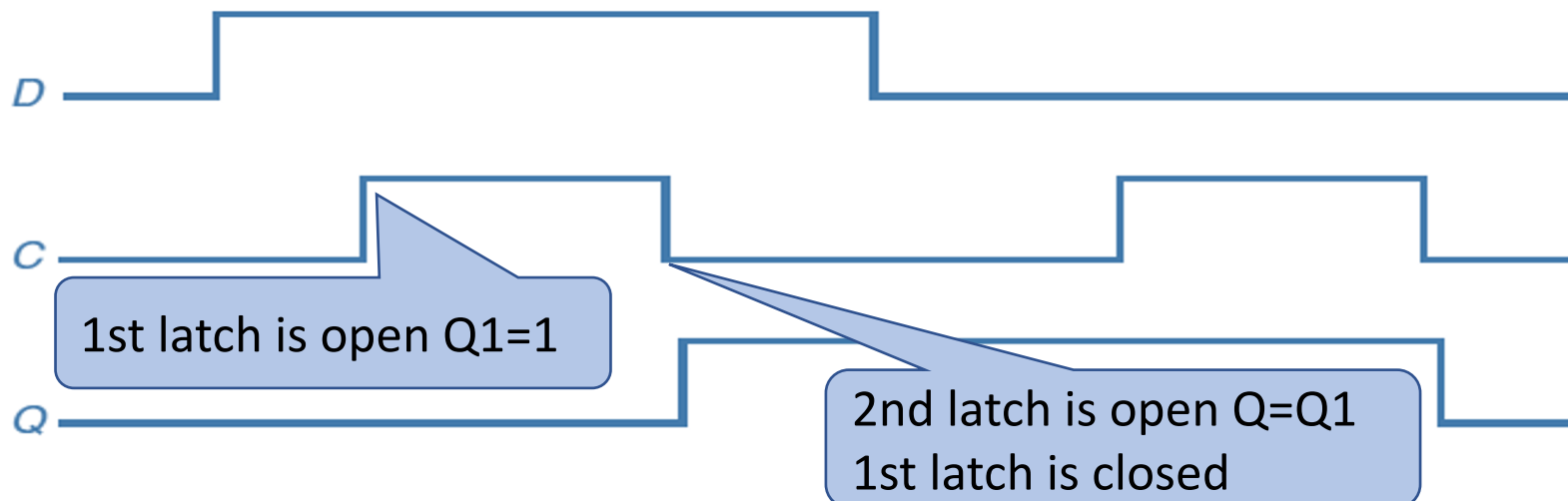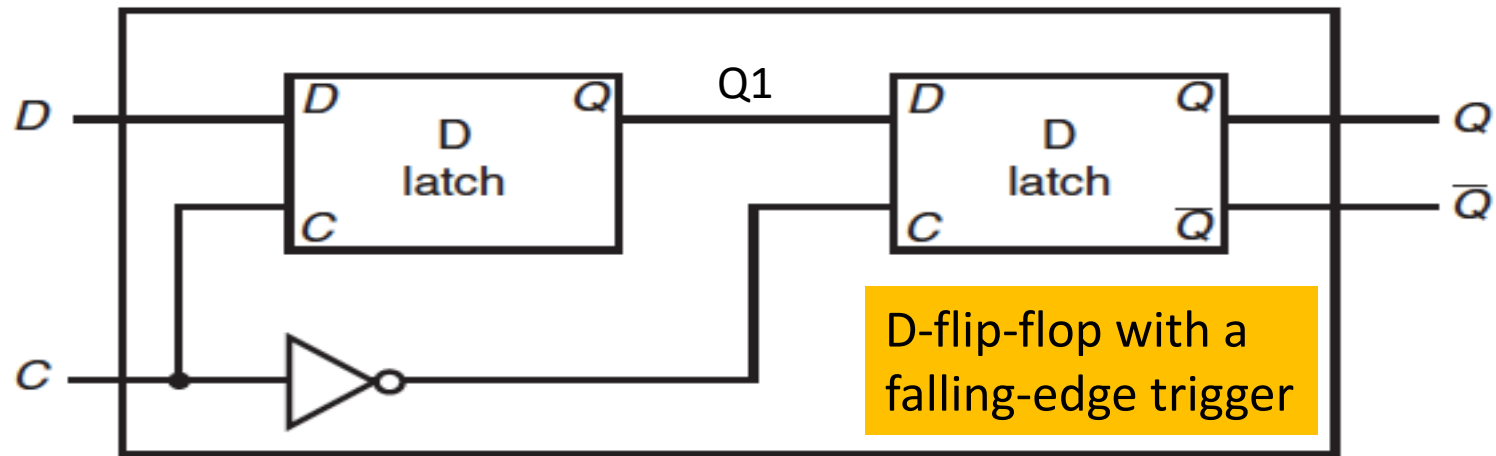
# Memory element: Flip-flop


- Flip-flop: state is changed only on (rising or falling) clock edge




# Finite State Machine

- Combinatorial logic → truth table
- Sequential logic → F(inite) S(tate) M(achine)
  - Input and current state determine next state and outputs

# Finite State Machine

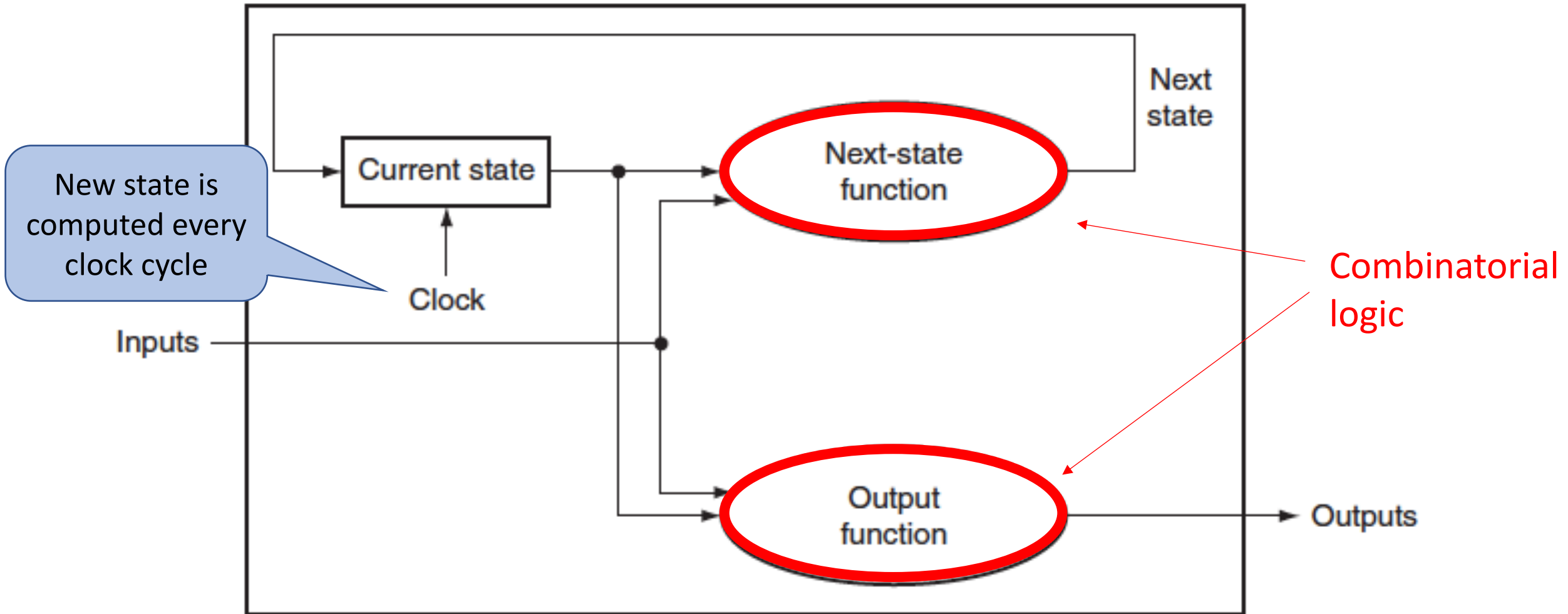

# FSM example: traffic light control

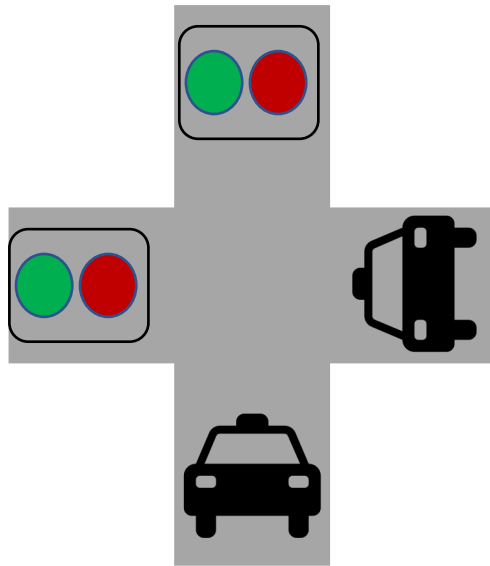

How many bits needed to represent state values?

State:

NSgreen: traffic light is green in N-S (red in E-W)

EWgreen: traffic light is green in E-W (red in N-S)

Inputs:

NScar: car detected in N-S



EWcar: car detected in E-W

Outputs:

NSlite: 1 if state=NSgreen

EWlite: 1 if state=EWgreen

# FSM example: traffic light control

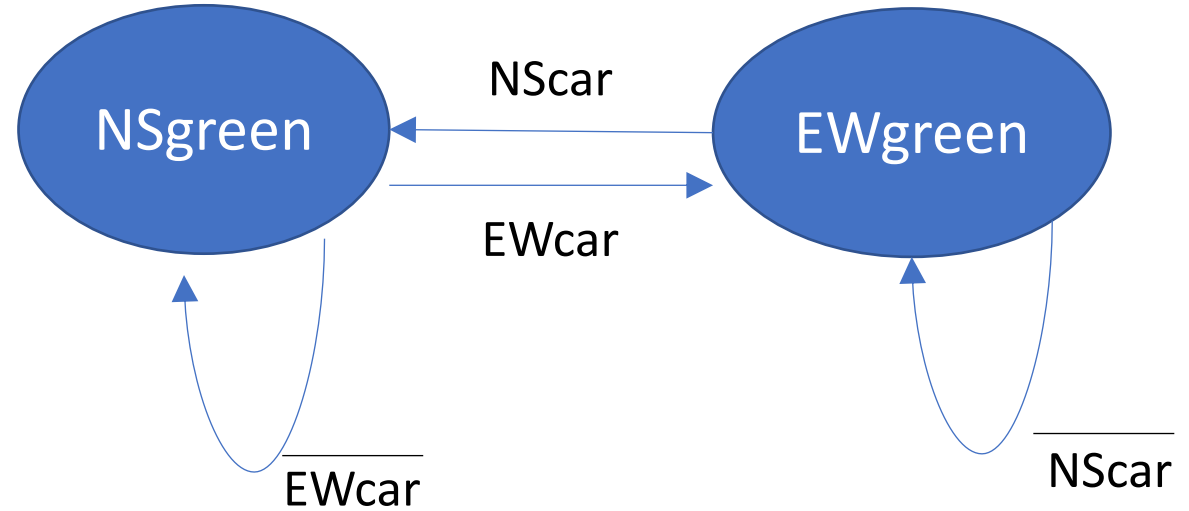 

Clock speed?


Clock cycles once every 30 seconds



# FSM example: traffic light

- FSM is determined by NextState function and Output function

	Inputs		
	NScar	EWcar	Next state
NSgreen	0	0	NSgreen
NSgreen	0	1	EWgreen
NSgreen	1	0	NSgreen
NSgreen	1	1	EWgreen
EWgreen	0	0	EWgreen
EWgreen	0	1	EWgreen
EWgreen	1	0	NSgreen
EWgreen	1	1	NSgreen

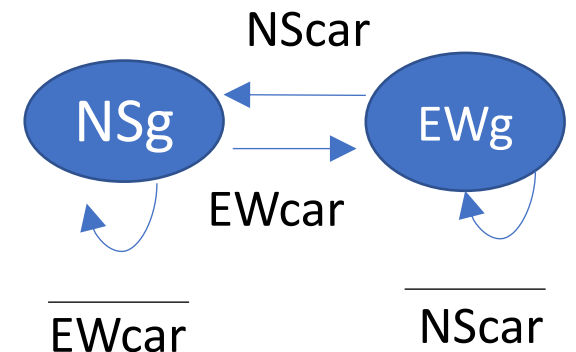

# FSM example: traffic light


- FSM is determined by NextState function and Output function

Current State	Inputs		Next state
	NScar	EWcar	
0 (Nsgreen)	0	0	0 (Nsgreen)
0 (Nsgreen)	0	1	1 (Ewgreen)
0 (Nsgreen)	1	0	0 (Nsgreen)
0 (Nsgreen)	1	1	1 (Ewgreen)
1 (Ewgreen)	0	0	1 (Ewgreen)
1 (Ewgreen)	0	1	1 (Ewgreen)
1 (Ewgreen)	1	0	0 (Nsgreen)
1 (Ewgreen)	1	1	0 (Nsgreen)

$$\begin{aligned}
 Next = & \overline{Curr} \cdot \overline{NScar} \cdot EWcar \\
 & + \overline{Curr} \cdot NScar \cdot EWcar \\
 & + Curr \cdot \overline{NScar} \cdot \overline{EWcar} \\
 & + Curr \cdot \overline{NScar} \cdot EWCar
 \end{aligned}$$
 
# FSM traffic light: next state function

$$Next = \overline{Curr} \cdot EWcar + Curr \cdot \overline{NScar}$$




# FSM traffic light: output function

		Outputs	
		NSlite	EWlite
0	NSgreen	1	0
1	EWgreen	0	1

$$\text{NSLite} = \overline{\text{Curr}}$$


$$\text{EWLite} = \text{Curr}$$

# FSM traffic light: output function

 

# Another FSM example: Electronic eye


State transition diagram?

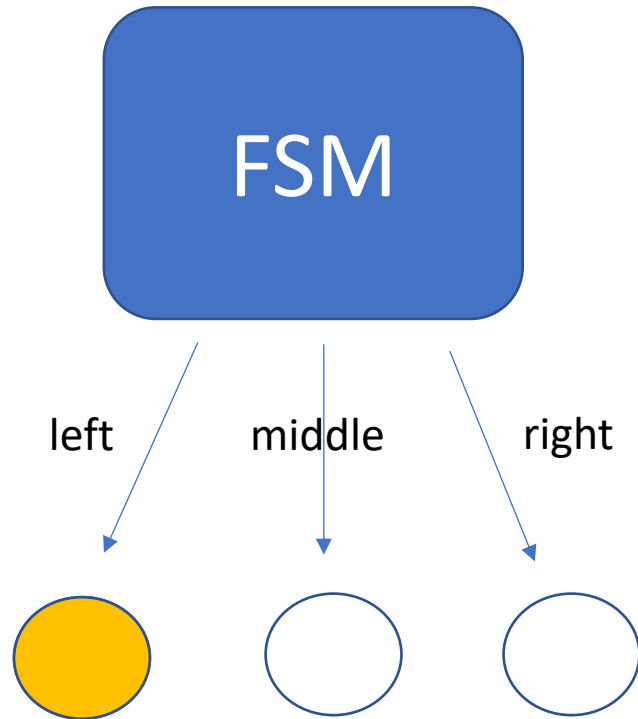


Lights are lit from left to right, then right to left and so on
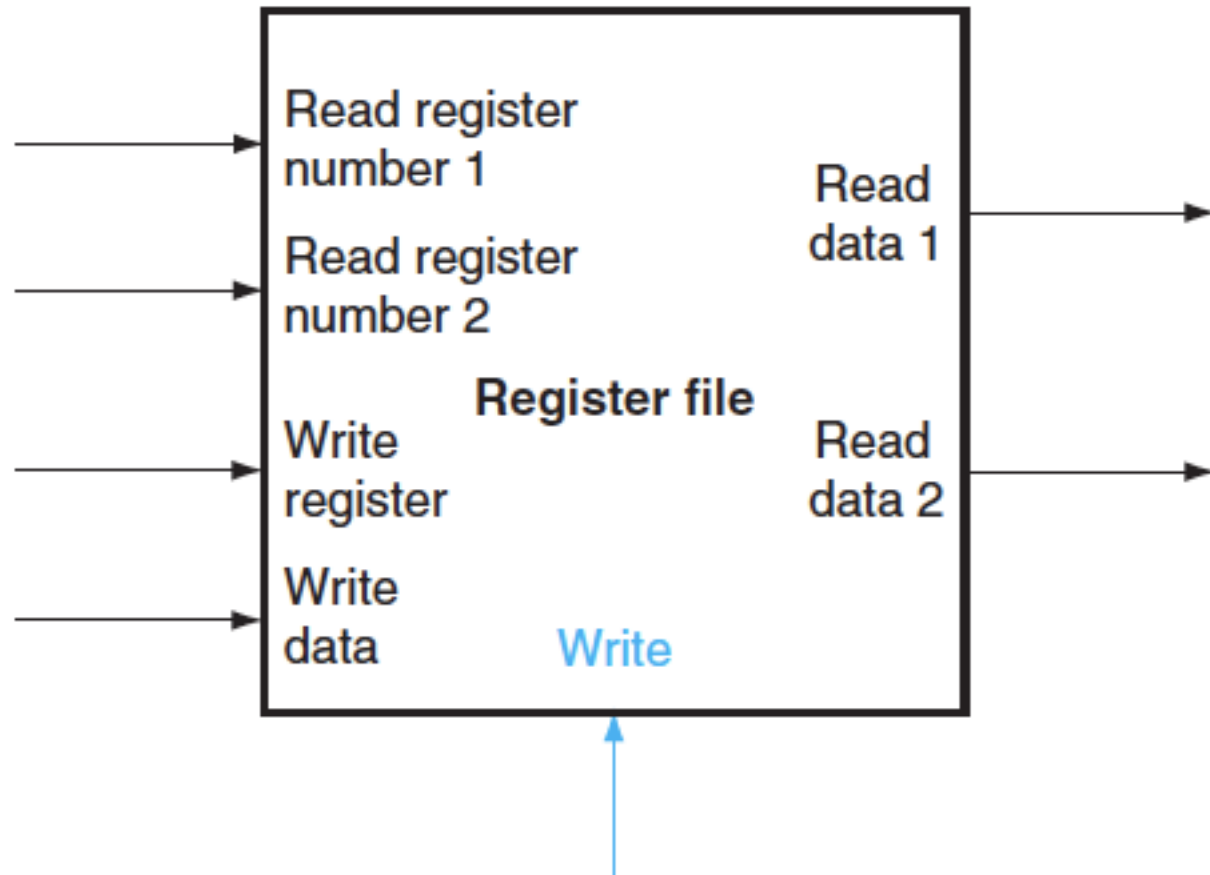
# Memory element: Register file

- Register file: a set of registers that can be read and written




😞 Why reading two registers at a time?

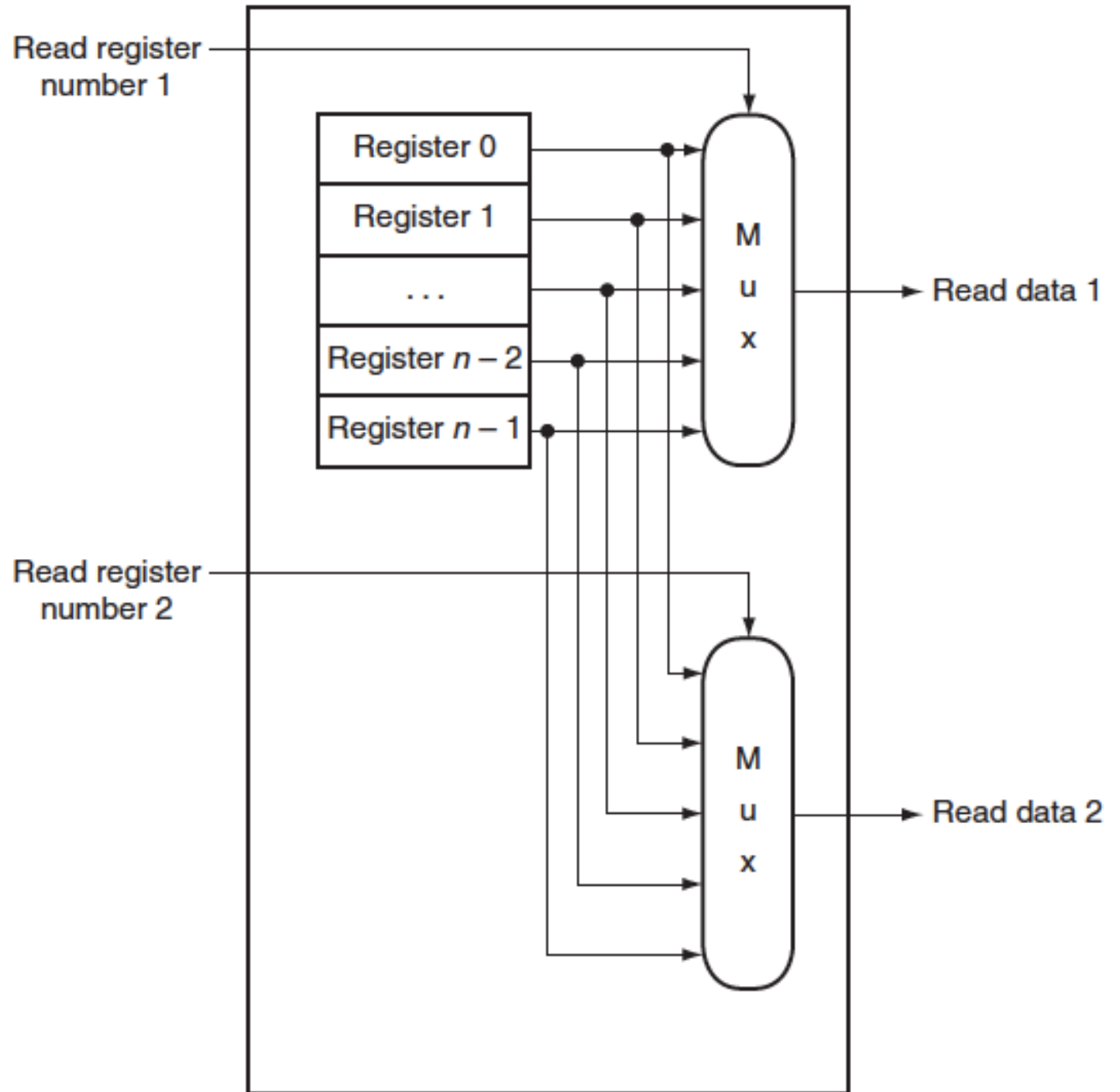

Clock signal is assumed and not drawn



Register file:  
Write

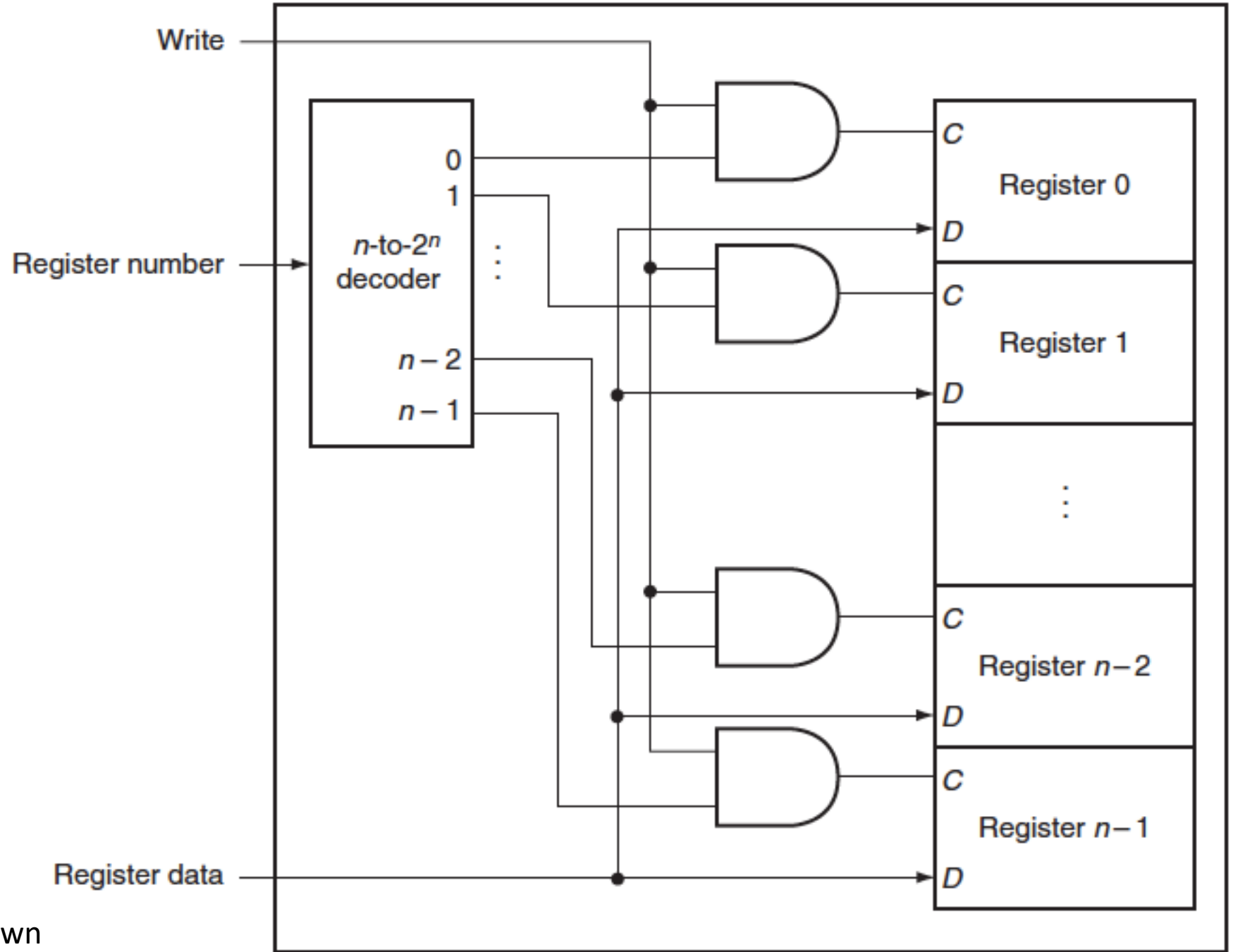

Clock signal is assumed and not drawn


# Register file

- What if the same register is read and written in the same clock cycle?
  - Return register value written in an earlier cycle
  - Write of new value occurs on the clock edge (at the end of the current cycle)
- Some register file can read value currently being written
  - Requires additional logic in the register file

# Summary

- Memory (state) elements
  - Requires a clock signal to know when to update state value
  - Unclocked S-R latch → Clocked D latch → Flip-flop
- Sequential logic
  - Finite state machine
  - Decompose into two CL functions
    - Next state function: compute next state value based on current state value and inputs
    - Output function: compute output based on current state value and inputs

# Happy Thanksgiving!

 

## Stay safe!